Feedback Amplifier Categories FEEDBACK TYPE AMPLIFIER TYPE AND GAIN DEFINITION

TARIF 11.2

Shunt-series

Series-series

INPUT-OUTPUT		
Series-shunt	Voltage amplifier: $A_{\nu} = \frac{\mathbf{v_0}}{\mathbf{v}}$	

Series-shunt	Voltage	amplifier:	$A_{\nu} =$	$\frac{\mathbf{v_o}}{\mathbf{v_i}}$	
	_				V

Series-shunt	Voltage amplifier: $A_v = \frac{3}{\mathbf{v_i}}$
Shunt-shunt	Transresistance amplifier: $A_{tr} = \frac{\mathbf{v_o}}{\mathbf{i}}$

Shunt-shunt	Shunt-shunt	Transresistance	amplifier:	A =	$\underline{\mathbf{v_o}}$
	Shunt-shunt			A_{tr} —	$\mathbf{i_i}$

Current amplifier: $A_i = \frac{\mathbf{i_0}}{\mathbf{i}}$

Transconductance amplifier: $A_{tc} = \frac{\mathbf{i_0}}{\mathbf{v_i}}$